

---

**CMPE 200**

## COMPUTER ARCHITECTURE

### Lecture 3 – The Processor – Single Clock

Bo Yu  
Computer Engineering Department  
SJSU

Adapted from Computer Organization and Design, 5<sup>th</sup> Edition, 4<sup>th</sup> edition, Patterson and Hennessy, MK  
and Computer Architecture – A Quantitative Approach, 4<sup>th</sup> edition, Patterson and Hennessy, MK

---

# Lecture 2 Key Concepts Review

---

## ■ Last Lecture

- **ISA - Language of the Computer:**
  - Instructions: Language of the computer
  - Different computer architectures
  - MIPS Architecture

# Lecture 2 Key Concepts Review

---

- MIPS Instruction Set
  - o a RISC instruction set architecture
  - o Interface between software and its hardware
  - o a computer's assembly language
  - o Current version MIPS32/64 release 6, MIPS32 is used as example throughout the book
  - o Instructions are encoded in binary (machine code)
- MIPS has a 32 x 32-bit register file (GPR)
  - o Use for frequently accessed data, faster than memory
  - o Numbered 0 to 31
  - o 32-bit data called a "word"
  - o MIPS instructions are encoded as 32-bit instruction words, all instructions a single size
  - o 3 types of MIPS instruction set format: R-type, I-type, J-type
  - o MIPS is big endian (most significant byte at least address of a word)
- Memory Operands
  - o Main memory: Arrays, structures, dynamic data
  - o Load (memory to register), store (register to memory)
  - o Memory is byte (8-bit) addressed, address must be a multiple of 4 for words aligned in memory
- Binary signed and unsigned number
  - o Two's complement representation: leading 0s mean positive, leading 1s mean negative
  - o 32bits (MSB-sign bit):  $(d_{31} \times 2^{31}) + (d_{30} \times 2^{30}) + (d_{29} \times 2^{29}) + \dots + (d_1 \times 2^1) + (d_0 \times 2^0)$
- Design Principle 1: Simplicity favors regularity
  - o Regularity makes implementation simpler
  - o Simplicity enables higher performance at lower cost
- Design Principle 2: Smaller is faster
  - o c.f. main memory: millions of locations
- Design Principle 3: Good design demands good compromises
  - o Keep all instructions the same length, different formats for different instructions
- Design Principle 4: Making the common case fast

# Lecture 2 Key Concepts Review

- MIPS 32 General Purpose Registers (GPR)

Register Number	Conventional Name	Usage
\$0	\$zero	Hard-wired 0
\$1	\$at	Reserved by assembler to handle large constants
\$2-\$3	\$v0, \$v1	Return values from functions
\$4 - \$7	\$a0 - \$a3	Arguments to functions, not preserved by subprograms
\$8 - \$15	\$t0 - \$t7	Temporary data, not preserved by subprograms
\$16 - \$23	\$s0 - \$s7	Saved registers, preserved by subprograms
\$24 - \$25	\$t8 - \$t9	More temporary data, not preserved by subprograms
\$26 - \$27	\$k0 - \$k1	Reserved by kernel. Do not use.
\$28	\$gp	Global Area Pointer (base of global data segment)
\$29	\$sp	Stack Pointer
\$30	\$fp	Frame Pointer
\$31	\$ra	Return Address

- MIPS Instruction Format


Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	op	rs	rt	address/immediate			Transfer, branch, imm. format
J-format	op	target address					Jump instruction format

- MIPS Instruction Classes and Assembly Language


Instruction class	MIPS examples	HLL correspondence
Arithmetic	add, sub, addi	Arithmetic operations
Data transfer	lw, sw, lh, lhu, sh, lb, lbu, sb	References to data structure, etc.
Logical	And, or, nor, andi, ori, sll, srl	Logical operations
Conditional branch	Beq, bne, slt, sltu, slti, sltiu	If statements and loops
Unconditional jump	J, jr, jal	Procedure calls, returns, case/switch statements

## Lecture 2: Instructions: Language of the Computer

Word address must be a multiple of 4

 

Big Endian vs. Little Endian

 

## Lecture 2 Key Concepts Review

- MIPS instruction encoding

Instruction	Format	op	rs	rt	rd	shamt	funct	address
add	R	0	reg	reg	reg	0	32 <sub>ten</sub>	n.a.
sub (subtract)	R	0	reg	reg	reg	0	34 <sub>ten</sub>	n.a.
add immediate	I	8 <sub>ten</sub>	reg	reg	n.a.	n.a.	n.a.	constant
lw (load word)	I	35 <sub>ten</sub>	reg	reg	n.a.	n.a.	n.a.	address
sw (store word)	I	43 <sub>ten</sub>	reg	reg	n.a.	n.a.	n.a.	address

- MIPS machine language

### MIPS machine language

Name	Format	Example						Comments
add	R	0	18	19	17	0	32	add \$s1,\$s2,\$s3
sub	R	0	18	19	17	0	34	sub \$s1,\$s2,\$s3
addi	I	8	18	17	100			addi \$s1,\$s2,100
lw	I	35	18	17	100			lw \$s1,100(\$s2)
sw	I	43	18	17	100			sw \$s1,100(\$s2)
Field size		6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	R	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	I	op	rs	rt	address			Data transfer format

## Lecture 2 Key Concepts Review

---

- MIPS R-format Example

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

add \$t0, \$s1, \$s2

special	\$s1	\$s2	\$t0	0	add
---------	------	------	------	---	-----

0	17	18	8	0	32
---	----	----	---	---	----

000000	10001	10010	01000	00000	100000
--------	-------	-------	-------	-------	--------

$00000010001100100100000000100000_2 = 02324020_{16}$

## Lecture 2 Key Concepts Review

- MIPS I-format Instructions

op	rs	rt	constant or address
6 bits	5 bits	5 bits	16 bits

- Immediate arithmetic and load/store instructions
  - ❖ rt: destination or source register number
  - ❖ Constant:  $-2^{15}$  to  $+2^{15} - 1$
  - ❖ Address: offset added to base address in rs

- Example of translating MIPS Assembly Language into Machine Language:

**A[300] = h + A[300];** \$t1 has base address of array A, \$s2 corresponds to h

The above assignment statement is compiled into:

Assembly Language  $\Rightarrow$

```
lw    $t0,1200($t1) # Temporary reg $t0 gets A[300]
add   $t0,$s2,$t0   # Temporary reg $t0 gets h + A[300]
sw    $t0,1200($t1) # Stores h + A[300] back into A[300]
```

Machine Language Instructions  $\Rightarrow$

Op	rs	rt	rd	address/ shamt	funct
35	9	8		1200	
0	18	8	8	0	32
43	9	8		1200	

Machine Binary Code  $\Rightarrow$

100011	01001	01000	0000 0100 1011 0000		
000000	10010	01000	01000	00000	100000
101011	01001	01000	0000 0100 1011 0000		



## Lecture 2: Instructions: Language of the Computer

### ■ Binary signed and unsigned number

- Representation of Signed numbers

- Sign and magnitude: Add a separate sign represented in a single bit ✖
- Two's Complement Representation (every computer uses today)
  - leading 0s mean positive, leading 1s mean negative
- 32bits (MSB-sign bit):  $(d_{31} \times 2^{31}) + (d_{30} \times 2^{30}) + (d_{29} \times 2^{29}) + \dots + (d_1 \times 2^1) + (d_0 \times 2^0)$

- Signed numbers

0000 0000 0000 0000 0000 0000 0000 0000<sub>two</sub> = 0<sub>ten</sub>

0000 0000 0000 0000 0000 0000 0000 0001<sub>two</sub> = 1<sub>ten</sub>

0000 0000 0000 0000 0000 0000 0000 0010<sub>two</sub> = 2<sub>ten</sub>

.....  
0111 1111 1111 1111 1111 1111 1111 1101<sub>two</sub> = 2,147,483,645<sub>ten</sub> =  $(2^{31}-3)$

0111 1111 1111 1111 1111 1111 1111 1110<sub>two</sub> = 2,147,483,646<sub>ten</sub> =  $(2^{31}-2)$

0111 1111 1111 1111 1111 1111 1111 1111<sub>two</sub> = 2,147,483,647<sub>ten</sub> =  $(2^{31}-1)$

**1000 0000 0000 0000 0000 0000 0000 0000<sub>two</sub> = -2,147,483,648<sub>ten</sub> =  $(-2^{31})$**

1000 0000 0000 0000 0000 0000 0000 0001<sub>two</sub> = -2,147,483,647<sub>ten</sub> =  $(2^{31}+1)$

1000 0000 0000 0000 0000 0000 0000 0010<sub>two</sub> = -2,147,483,646<sub>ten</sub> =  $(2^{31}+2)$

.....  
1111 1111 1111 1111 1111 1111 1111 1101<sub>two</sub> = -3<sub>ten</sub>

1111 1111 1111 1111 1111 1111 1111 1110<sub>two</sub> = -2<sub>ten</sub>

1111 1111 1111 1111 1111 1111 1111 1111<sub>two</sub> = -1<sub>ten</sub>

## Lecture 2: Instructions: Language of the Computer

---

### ■ Signed Negation

#### ■ Complement and add 1

- Complement means  $1 \rightarrow 0, 0 \rightarrow 1$

$$x + \bar{x} = 1111 \dots 111_2 = -1$$

$$\bar{x} + 1 = -x$$

#### ■ Example: negate +2

- $+2 = 0000\ 0000 \dots 0010_2$
- $-2 = 1111\ 1111 \dots 1101_2 + 1$   
 $= 1111\ 1111 \dots 1110_2$

## Lecture 2: Instructions: Language of the Computer

---

### ■ Hexadecimal

#### ■ Base 16

- Compact representation of bit strings
- 4 bits per hex digit

0	0000	4	0100	8	1000	c	1100
1	0001	5	0101	9	1001	d	1101
2	0010	6	0110	a	1010	e	1110
3	0011	7	0111	b	1011	f	1111

#### ■ Example: eca8 6420

- 1110 1100 1010 1000 0110 0100 0010 0000

## Lecture 2 Key Concepts Review

---

### ■ Logical Operations

- Instructions for bitwise manipulation
- Useful for extracting and inserting groups of bits in a word

Logical Operations	C Operators	Java Operators	MIPS Instructions
Shift left logical	<<	<<	sll
Shift right logical	>>	>>>	srl
Bit-by-bit AND	&	&	and, andi
Bit-by-bit OR			or, ori
Bit-by-bit NOR	~	~	nor

## Lecture 2 Key Concepts Review

---

### ■ Shift Operations

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

- shamt: how many positions to shift
- Shift left logical
  - Shift left and fill with 0 bits
  - sll by  $i$  bits multiplies by  $2^i$
- Shift right logical
  - Shift right and fill with 0 bits
  - srl by  $i$  bits divides by  $2^i$  (unsigned only)

## Lecture 2 Key Concepts Review

---

### ■ Conditional Operations


- Branch to a labeled instruction if a condition is true
  - Otherwise, continue sequentially
- `beq rs, rt, L1`
  - if (`rs == rt`) branch to instruction labeled L1;
- `bne rs, rt, L1`
  - if (`rs != rt`) branch to instruction labeled L1;
- `j L1`
  - unconditional jump to instruction labeled L1

## Lecture 2 Key Concepts Review

---
 
### ■ Basic Blocks

- C code:
- A basic block is a sequence of instructions with
  - No embedded branches (except at end)
  - No branch targets (except at beginning)



- A compiler identifies basic blocks for optimization
- An advanced processor can accelerate execution of basic blocks

## Lecture 2 Key Concepts Review

---

### ■ More Conditional Operations

- Set result to 1 if a condition is true
  - Otherwise, set to 0
- `slt rd, rs, rt`
  - if ( $rs < rt$ )  $rd = 1$ ; else  $rd = 0$ ;
- `slti rt, rs, constant`
  - if ( $rs < \text{constant}$ )  $rt = 1$ ; else  $rt = 0$ ;
- Use in combination with `beq`, `bne`  
`slt $t0, $s1, $s2` # if ( $\$s1 < \$s2$ )  
`bne $t0, $zero, L` # branch to L



## Lecture 2 Key Concepts Review

---

### ■ Signed vs. Unsigned Comparison

- Signed comparison: slt, slti
- Unsigned comparison: sltu, sltui
- Example

○  $\$s0 = 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111$

○  $\$s1 = 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0001$

○ `slt $t0, $s0, $s1 # signed`

$$\diamond -1 < +1 \Rightarrow \$t0 = 1$$


○ `sltu $t0, $s0, $s1 # unsigned`

$$\diamond +4,294,967,295 > +1 \Rightarrow \$t0 = 0$$

# Lecture 2 Key Concepts Review
 
## ■ Memory Layout

- Text: program code
- Static data: global variables
  - e.g., static variables in C, constant arrays and strings
  - \$gp initialized to address allowing  $\pm$ offsets into this segment
  - \$sp  $\rightarrow$  starts at 7fff fffc, grows down towards data segment
  - \$gp  $\rightarrow$  starts at 1000 8000, moves using positive and negative 16-bit offset
  - Text Segment: MIPS machine code
  - Static data: starts at 1000 0000
  - Dynamic data: heap grows towards stack
- Dynamic data: heap
  - E.g., malloc in C, new in Java
- Stack: automatic storage



## Lecture 2 Key Concepts Review

### ■ Target Addressing Example

- Loop code from earlier example
  - Assume Loop at location 80000

Loop: sll	\$t1, \$s3, 2	80000	0	0	19	9	4	0
add	\$t1, \$t1, \$s6	80004	0	9	22	9	0	32
lw	\$t0, 0(\$t1)	80008	35	9	8	0		
bne	\$t0, \$s5, Exit	80012	5	8	21	2		
addi	\$s3, \$s3, 1	80016	8	19	19	1		
j	Loop	80020	2	20000				
Exit: ...		80024						


# Lecture 2 Key Concepts Review

## ■ Addressing Mode Summary

1. Immediate addressing




2. Register addressing

 


Registers

Register


3. Base addressing

 


Memory

 


4. PC-relative addressing

 


Memory

 

5. Pseudodirect addressing

 


Memory

 

## Lecture 2: Instructions: Language of the Computer

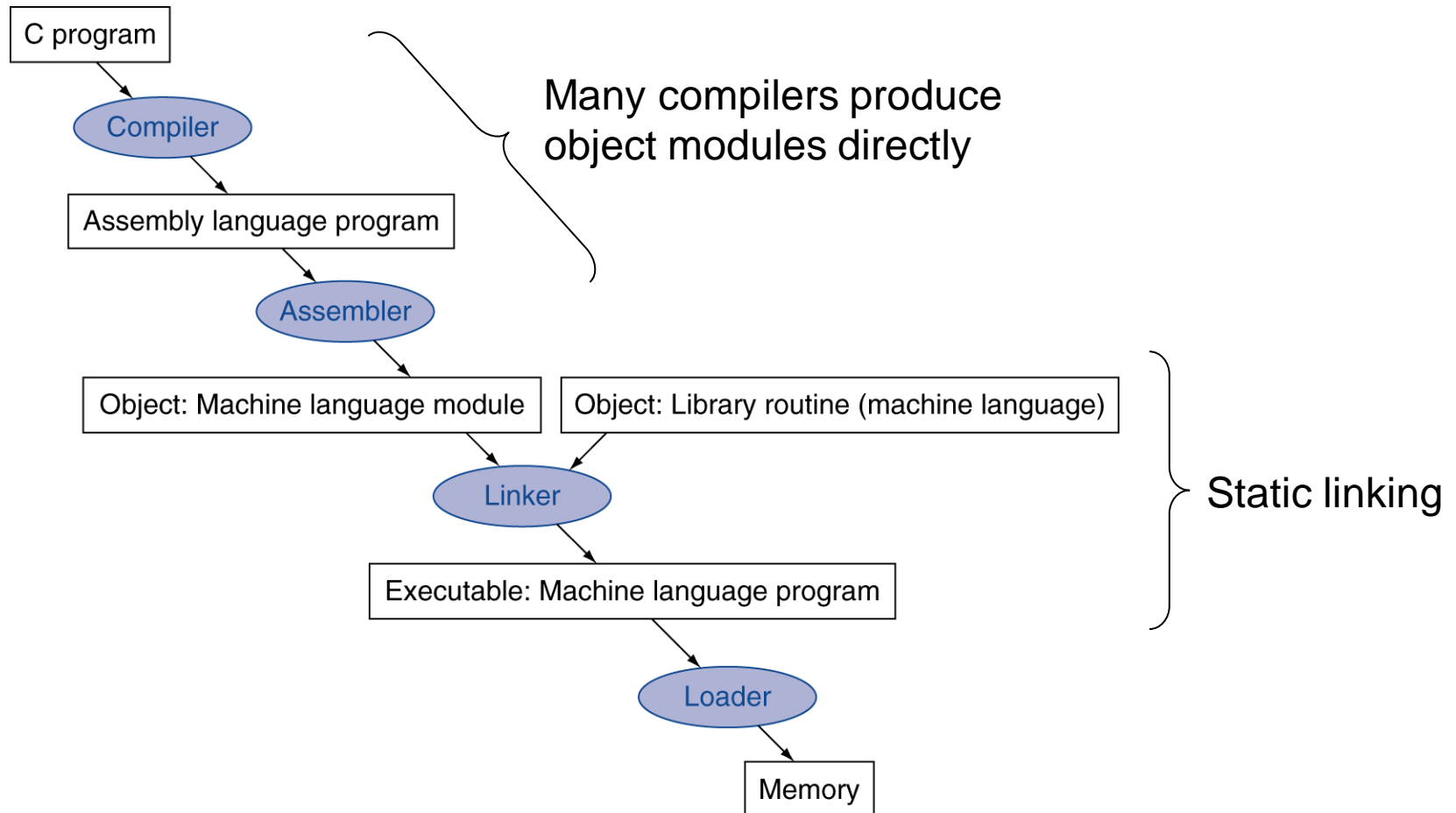
### ■ Four steps transforming a C program into a program running on a computer



## Lecture 3: The Processor
 
### ■ Today's Lecture (CH4.1-4.4):

- Datapath Design
  - **Single clock**
  - Pipelining - later
  - Hazards - later
  - Parallelism – ILP - later
- Control Unit Design
  - **Control Unit**
  - **Jumps**
  - CALL/RETURN - later
  - Exceptions - later



### ■ Two MIPS Implementations

- CPU performance factors
  - Instruction count: Determined by ISA and compiler
  - CPI and Cycle time: Determined by CPU hardware
- Simple MIPS Implementation
  - Single Clock Implementation
  - Fixed size instructions
  - Uses a subset of core MIPS instruction set
    - Memory reference: lw, sw
    - Arithmetic/logical: add, sub, and, or, slt
    - Control transfer: beq, j
- Pipelined MIPS Implementation

## Lecture 3: The Processor

---


### ■ Instruction Execution

- Instruction Fetch
  - PC  $\Rightarrow$  instruction memory  $\Rightarrow$  Instruction register
- Operand Read
  - Register Numbers  $\Rightarrow$  Register File
  - Read Registers
- Execute
  - ALU to calculate
    - Results for arithmetic operations
    - Data memory address for Load/Store
    - Branch target address (alternative implementation?)
- Access data memory for load/store
- Next Instruction
  - PC + target address for jumps or PC + 4



## Lecture 3: The Processor


### ■ CPU Overview

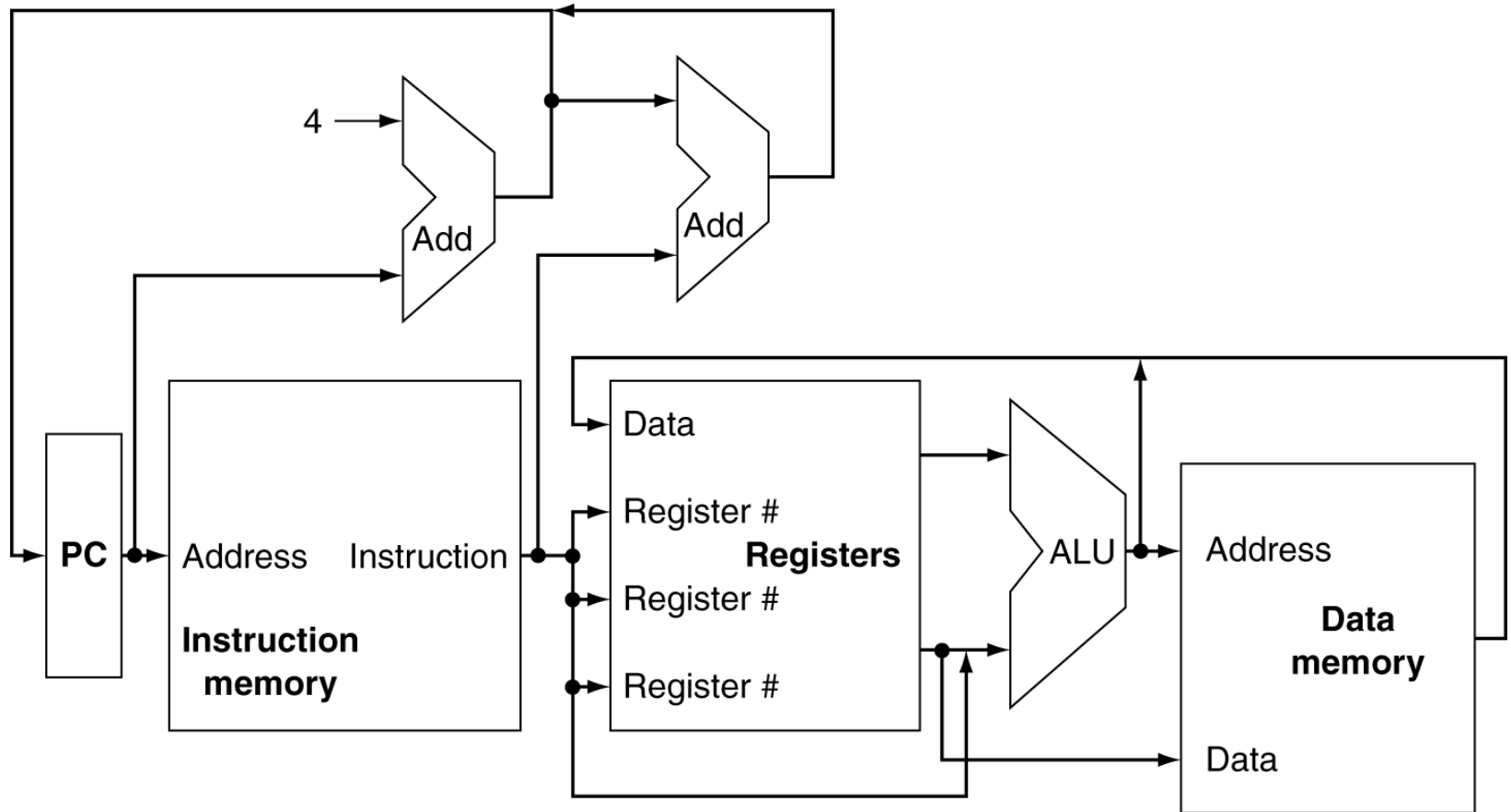

## Lecture 3: The Processor


### ■ Multiplexers

○ MUX points

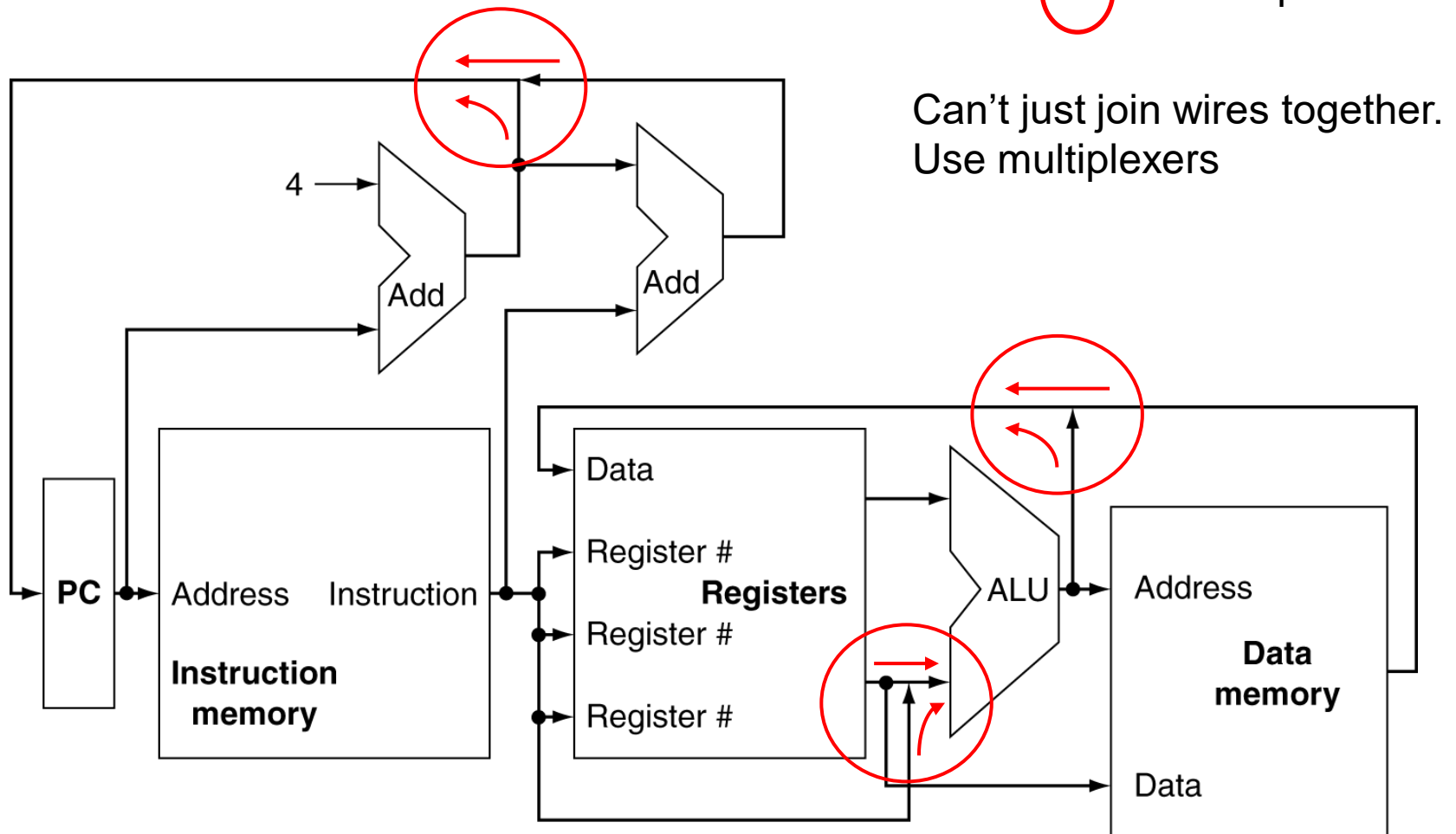

# Lecture 3: The Processor

## ■ Control

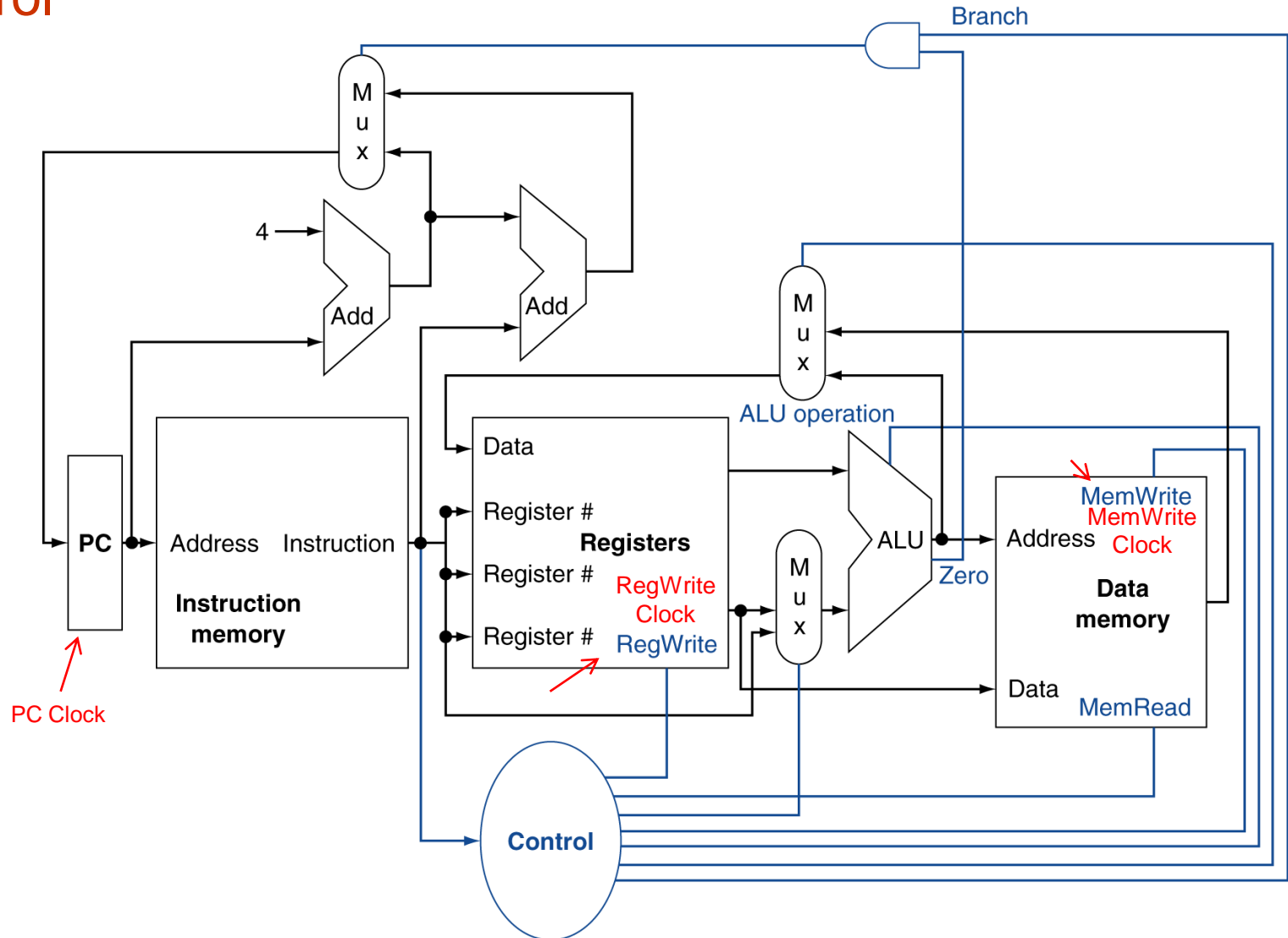


## Lecture 3: The Processor
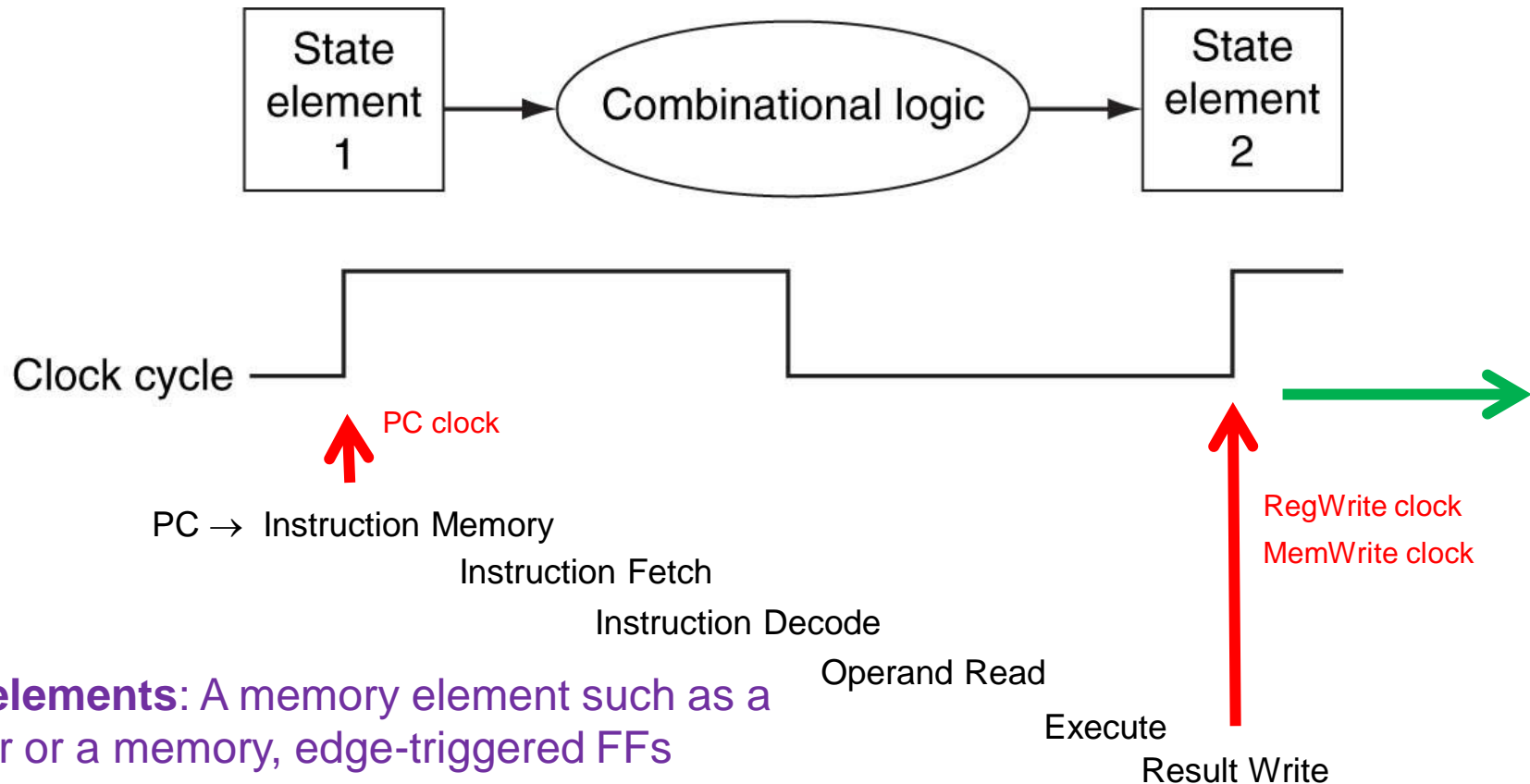
### ■ How it works – Single-Clock System

- **Clocking**


**Combinational logic:** An operational element such as an AND gate or an ALU


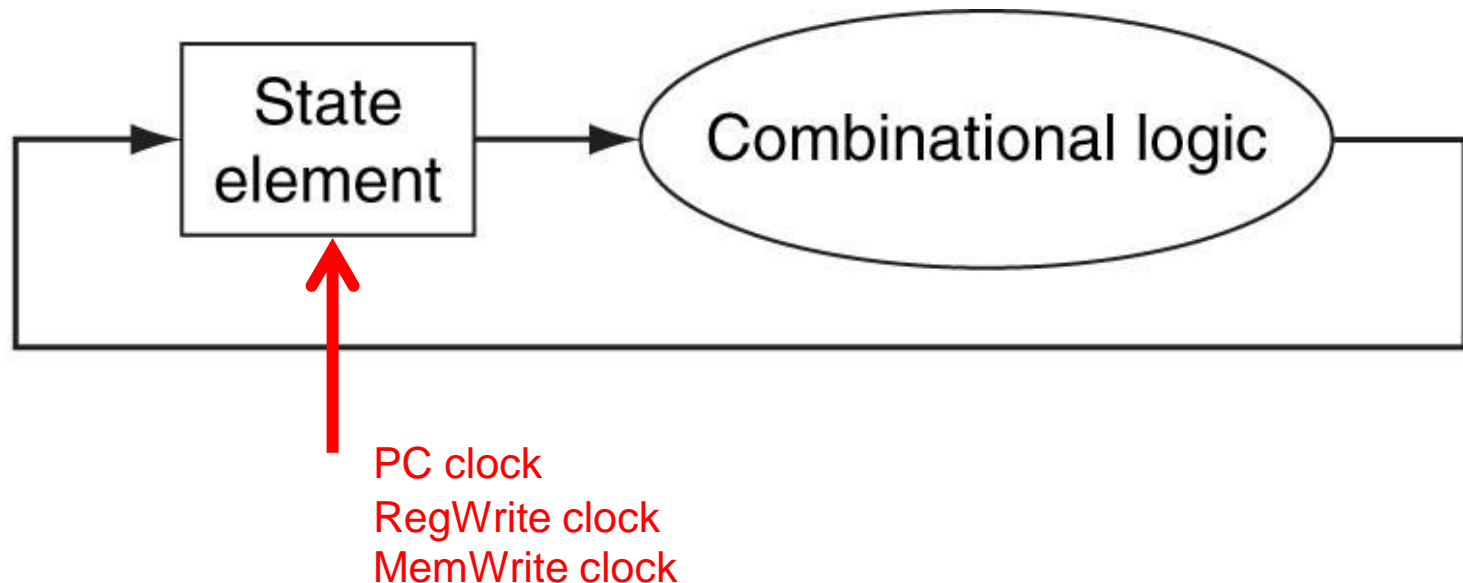
## Lecture 3: The Processor

---

- How it works – Single-Clock System
  - Clocking – continuous operation
  - Combinational logic transforms data during clock cycles
    - Between clock edges
    - Input from state elements, output to state element
    - Longest delay determines clock period



## Lecture 3: The Processor

---

### ■ Logic Design Basics


- **Information encoded in binary**
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- **Combinational element**
  - Operate on data
  - Output is a function of input
- **State (sequential) elements**
  - Store information

## Lecture 3: The Processor

### ■ Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 


- Adder

- $Y = A + B$

 

- Arithmetic/Logic Unit



- $Y = F(A, B)$

 

## Lecture 3: The Processor
  
### ■ Sequential Elements

- **Register: stores data in a circuit**
  - Uses a clock signal to determine when to update the stored value
  - Edge-triggered: update when Clk changes from 0 to 1







## Lecture 3: The Processor
  
### ■ Sequential Elements

- **Register with write control**
  - Only updates on clock edge when write control input is 1
  - Used when stored value is required later



## Lecture 3: The Processor


---

### ■ Building a Datapath

- **Datapath**
  - Elements that process data and addresses in the CPU
    - ❖ Registers, ALUs, mux's, memories, ...
- **We will build a MIPS datapath incrementally**
  - Refining the overview design

## Lecture 3: The Processor


- Data Path
  - Instruction Fetch

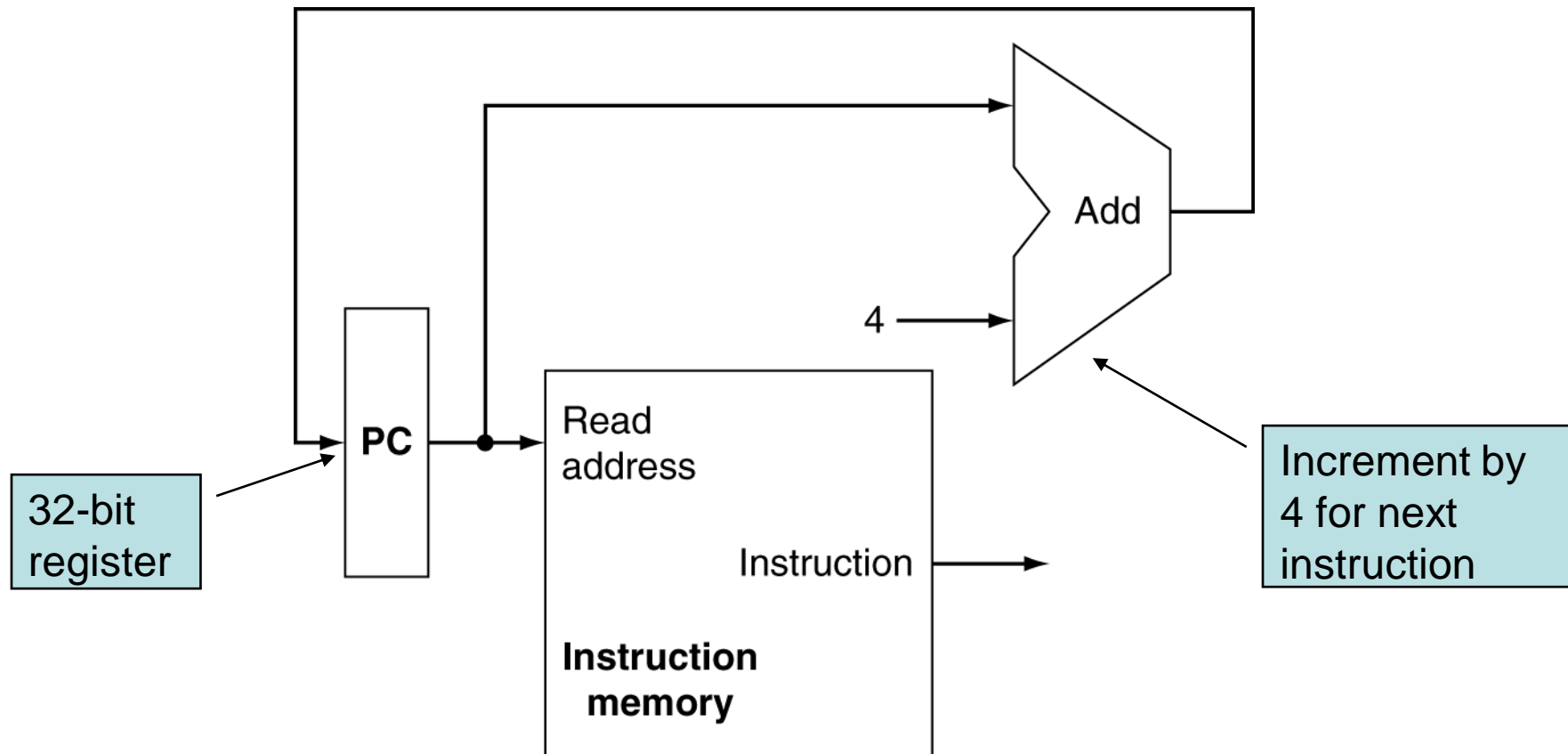

## Lecture 3: The Processor
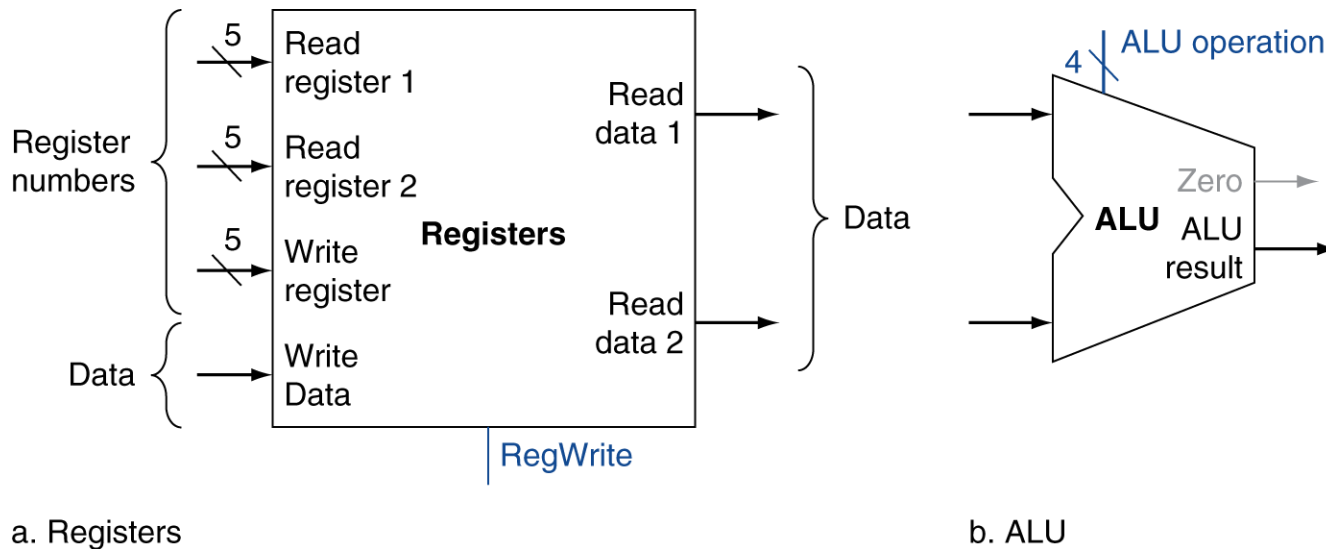
### ■ R-Format Instructions


- Read two register operands
- Perform arithmetic/logical operation
- Write register result



## Lecture 3: The Processor
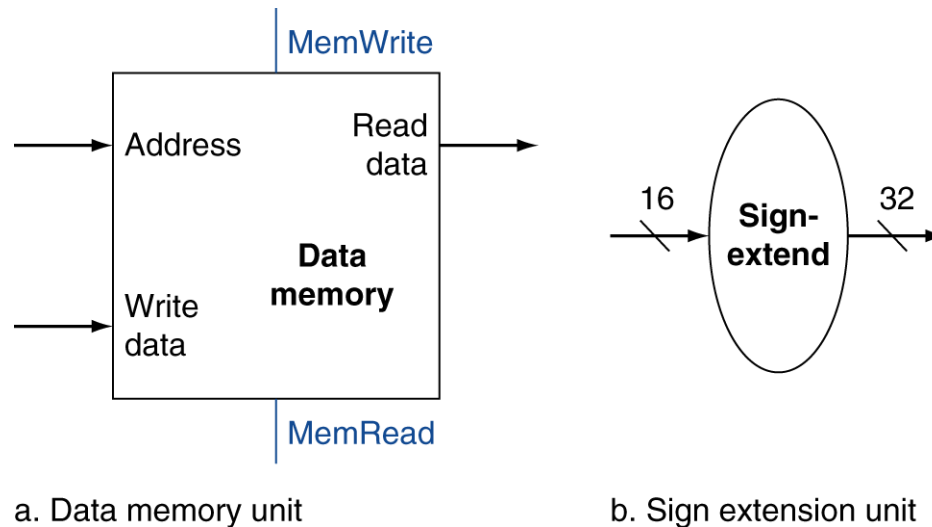
### ■ Load/Store (I-Format) Instructions

- Read register operands
- Calculate address using 16-bit offset
  - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory



# Lecture 3: The Processor

## ■ Branch Instructions


- **Read register operands**
- **Compare operands**
  - **Perform ALU op as required for condition testing**
  - **Use ALU, subtract and check Zero output**
- **Calculate target address based on the condition**
  - **Sign-extend displacement**
  - **Shift left 2 places (word displacement)**
  - **Add to PC + 4**
    - ❖ **Already calculated by instruction fetch**

## Examples (with RTL descriptions):

**BEQ** If [R(rs)==R(rt)] then PC = PC + signExt(Imm16) || 00  
else PC = PC + 4

## Lecture 3: The Processor

### ■ Branch Instructions

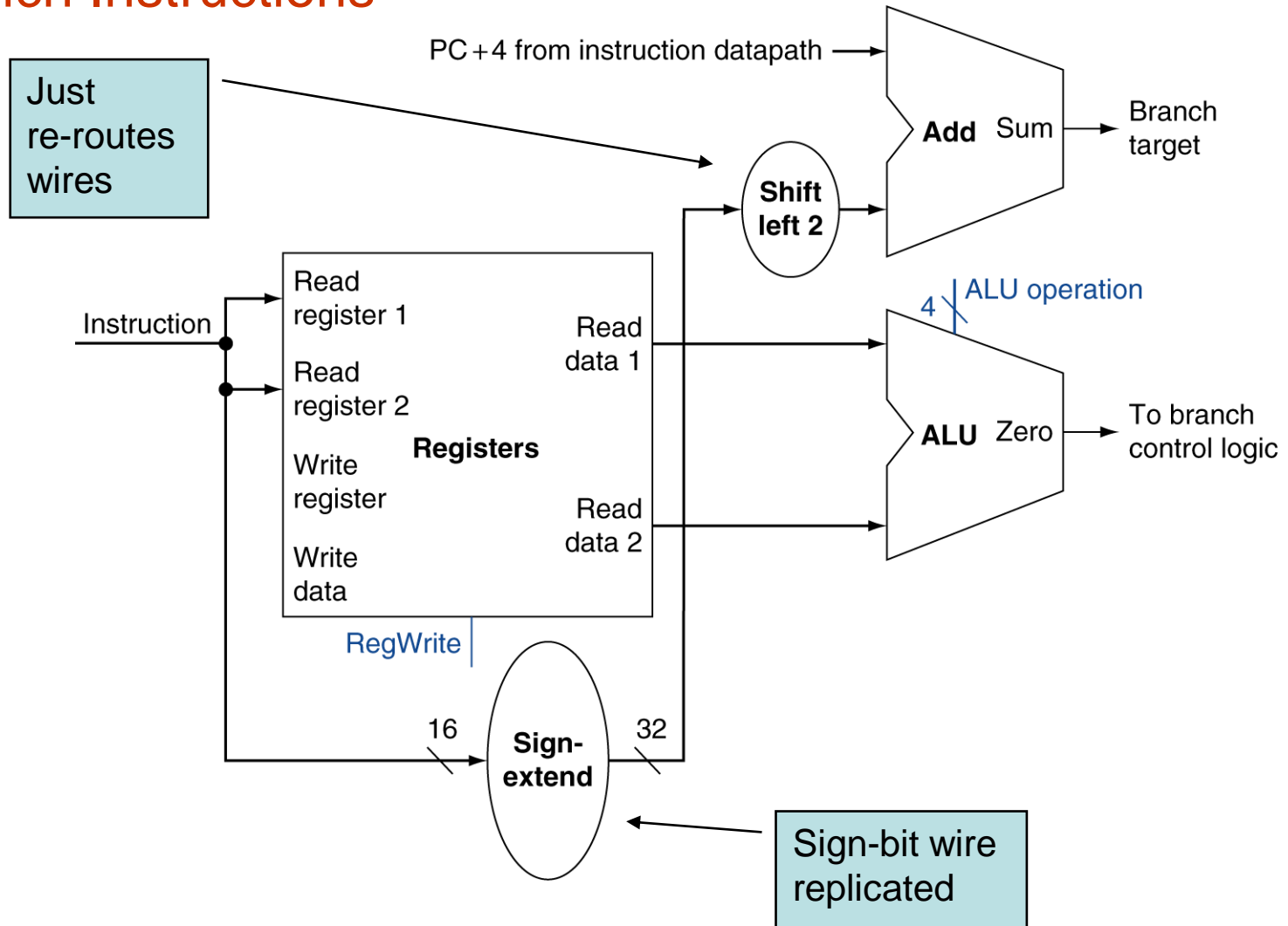

### ■ Composing the Elements

- **First-cut data path does an instruction in one clock cycle**
  - **Each datapath element can only do one function at a time**
  - **Hence, we need separate instruction and data memories**
- **Use multiplexers where alternate data sources are used for different instructions**



## Lecture 3: The Processor

### ■ R-Type and I-Type Datapath

- Read two register operands
- Perform arithmetic/logical operation
- Write register result


Examples (with RTL description):

**ADDU**     $R(rd) \leftarrow R(rs) + R(rt)$

**ADDI**     $R(rt) \leftarrow R(rs) + \text{signExt}(\text{Imm16})$

**OR**         $R(rd) \leftarrow R(rs) .\text{OR.} R(rt)$

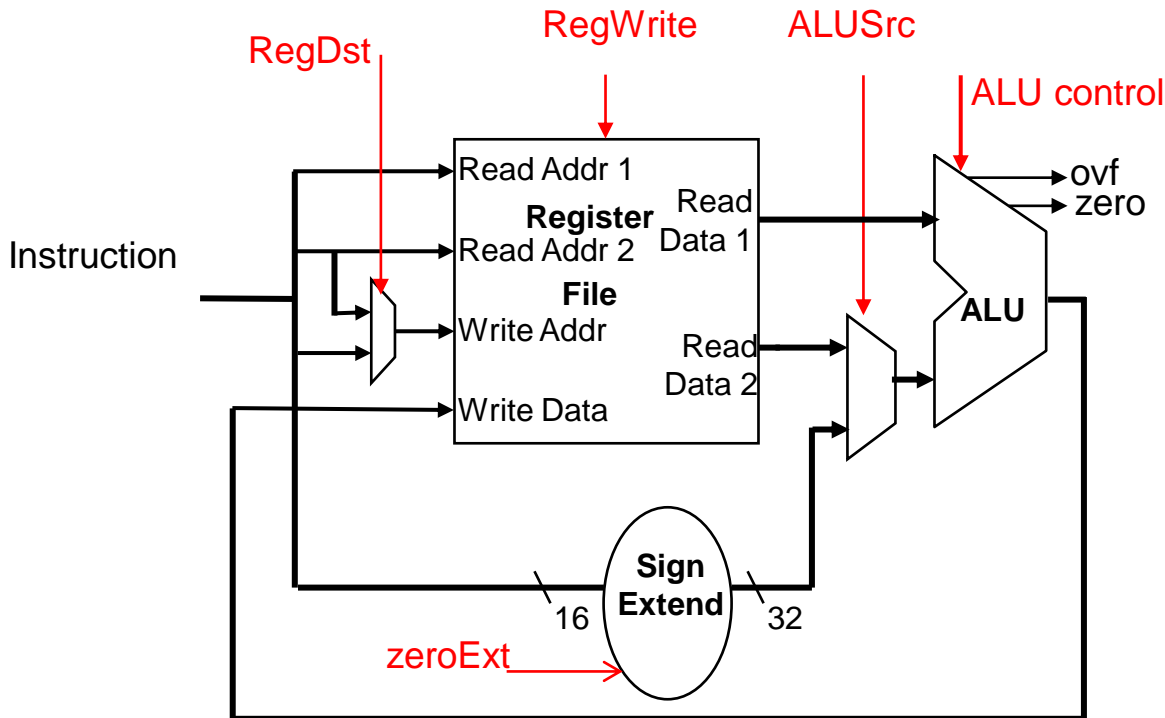**ORI**        $R(rt) \leftarrow R(rs) + \text{zeroExt}(\text{Imm16})$




## Lecture 3: The Processor

### ■ R-Type/Load/Store Datapath Examples (with RTL descriptions):

- Read register operands
- Calculate address using 16-bit offset
  - Use ALU, but sign-extend offset
- Load: Read memory, and update register
- Store: write register value to memory

**LD**  $R(rt) \leftarrow \text{Mem}[R(rs) + \text{signExt}(\text{Imm16})]$

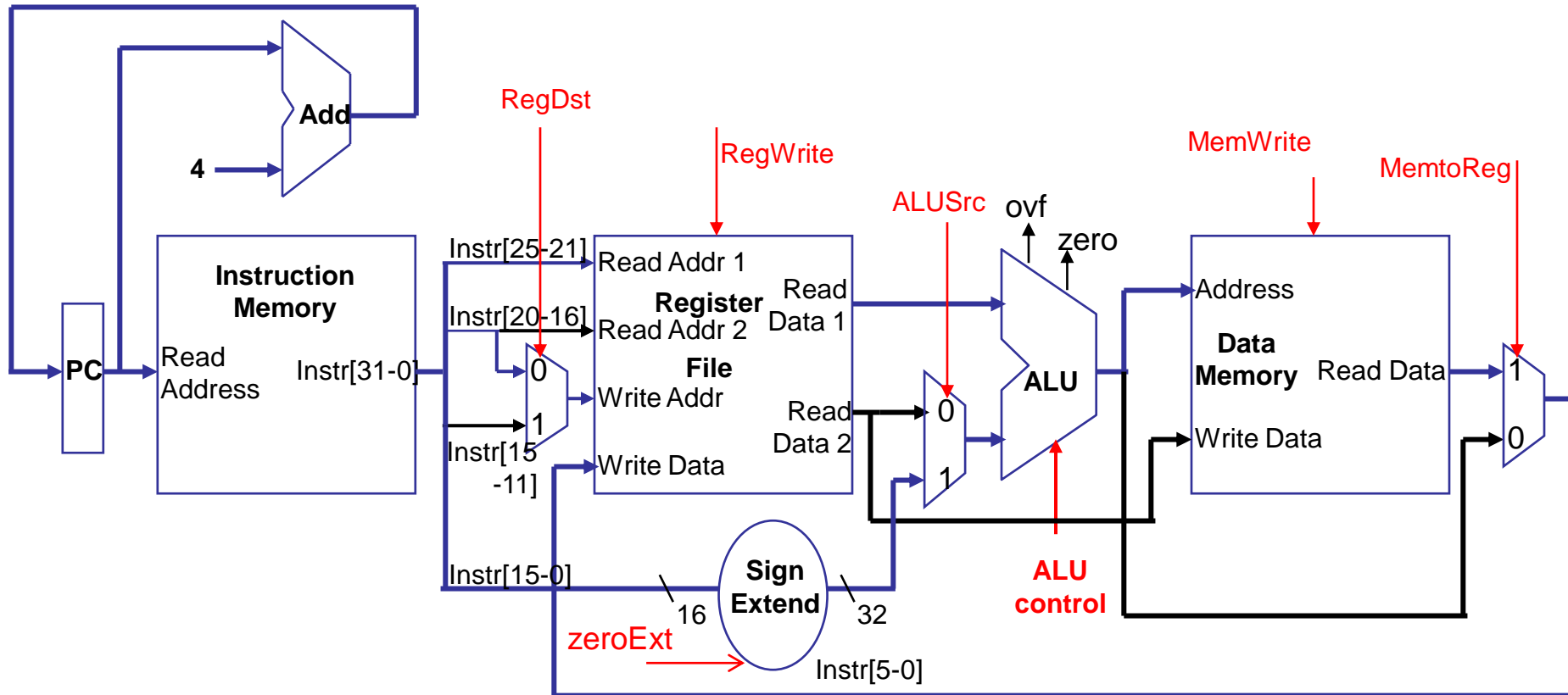**ST**  $\text{Mem}[R(rs) + \text{signExt}(\text{Imm16})] \leftarrow R(rt)$



## Lecture 3: The Processor


---

### ■ Polling: MemtoReg on LW

- Which of the following is correct for a load instruction?
  - a) MemtoReg should be set to cause the data from memory to be sent to the register file.
  - b) MemtoReg should be set to cause the correct register destination to be sent to the register file.
  - c) We don not care about the setting of MemtoReg for loads.

# Lecture 3: The Processor

## Full Datapath

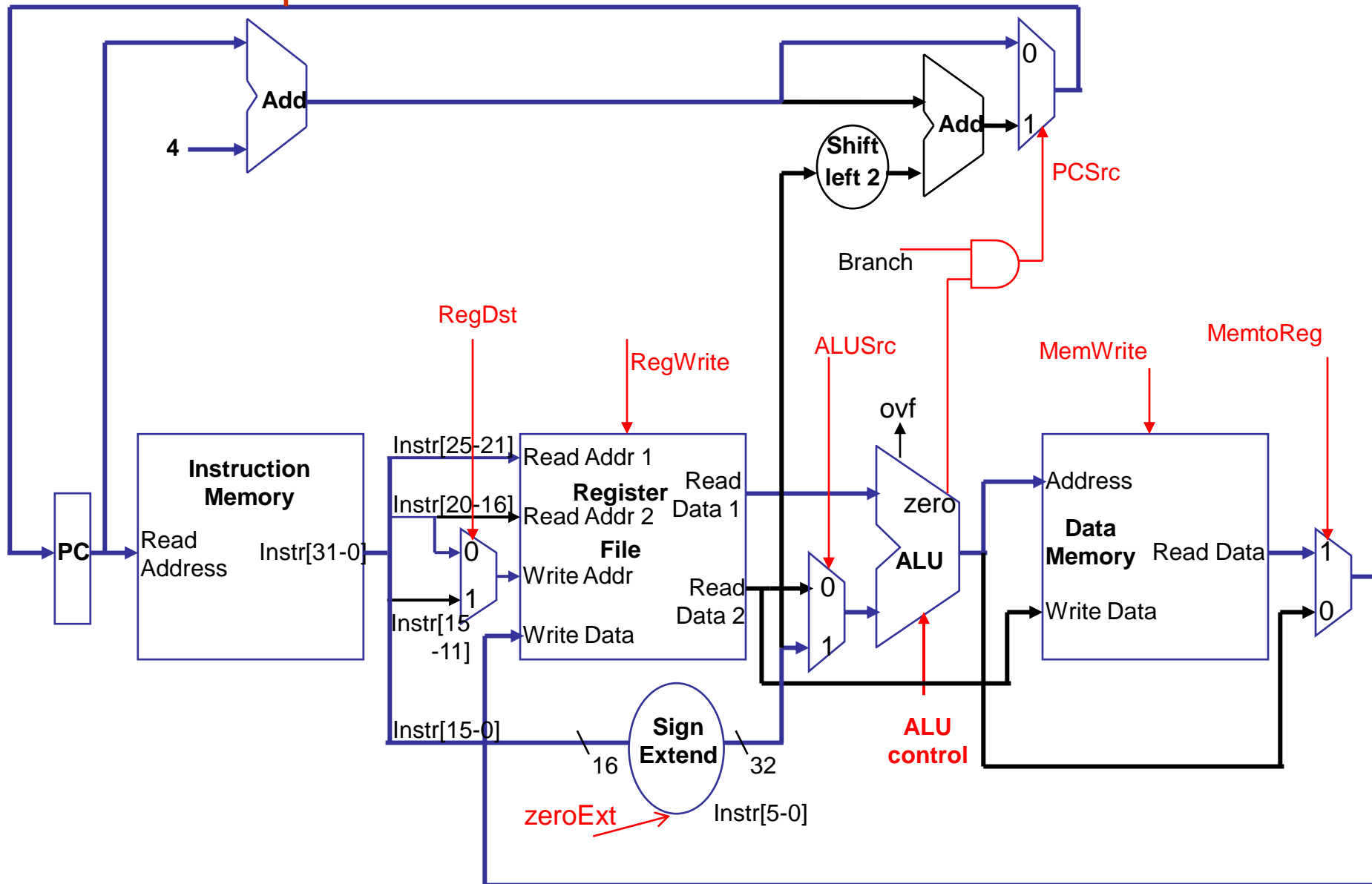

## Lecture 3: The Processor

---

### ■ ALU Control

- **ALU used for**

- **Load/Store: F = add (to compute the address)**
- **Branch: F = subtract**
- **R-type: F depends on funct field**

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

## Lecture 3: The Processor

### ■ ALU Control


- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control


opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111

## Lecture 3: The Processor


### ■ The Main Control Unit

 
#### ● Control signals derived from instruction




 



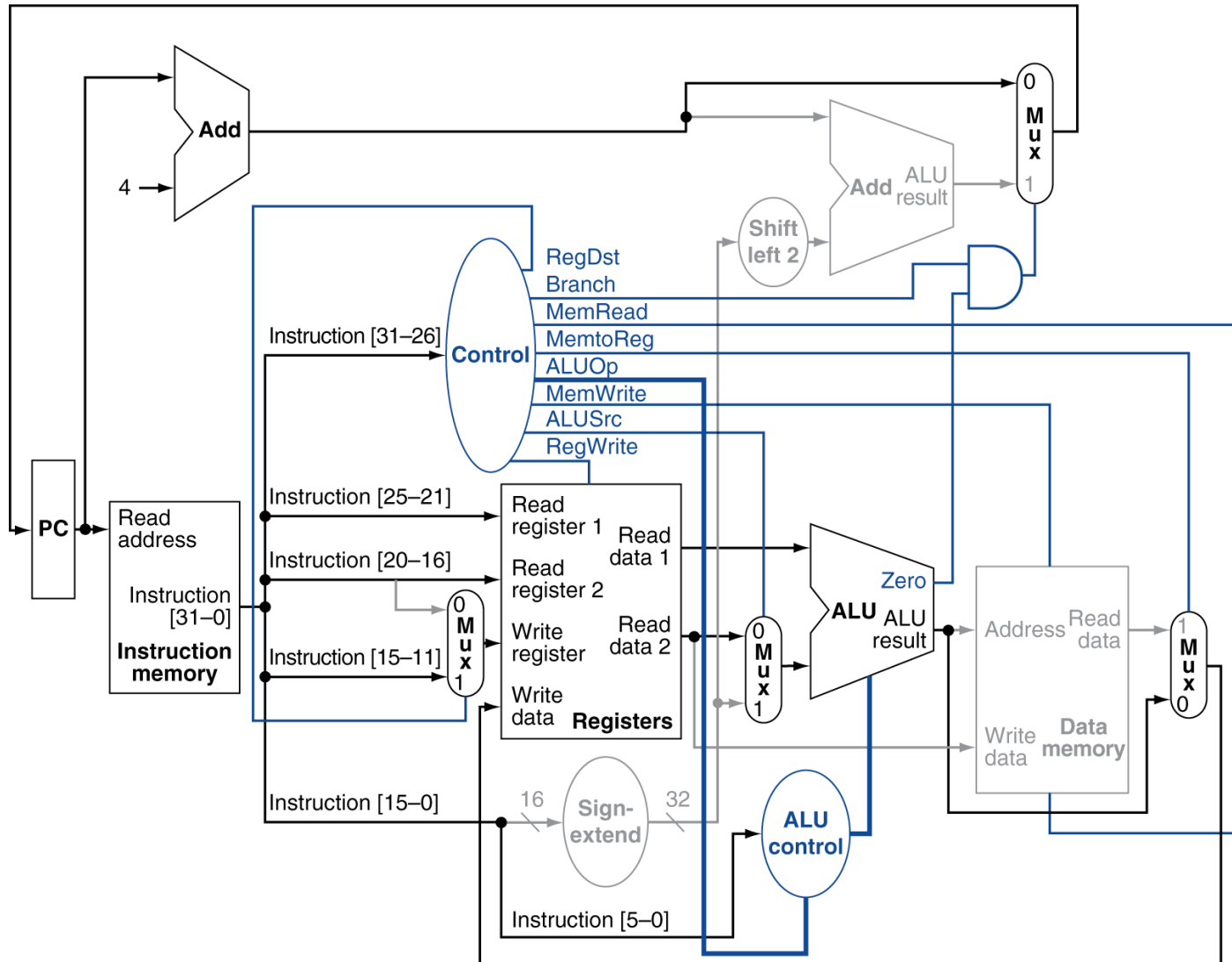


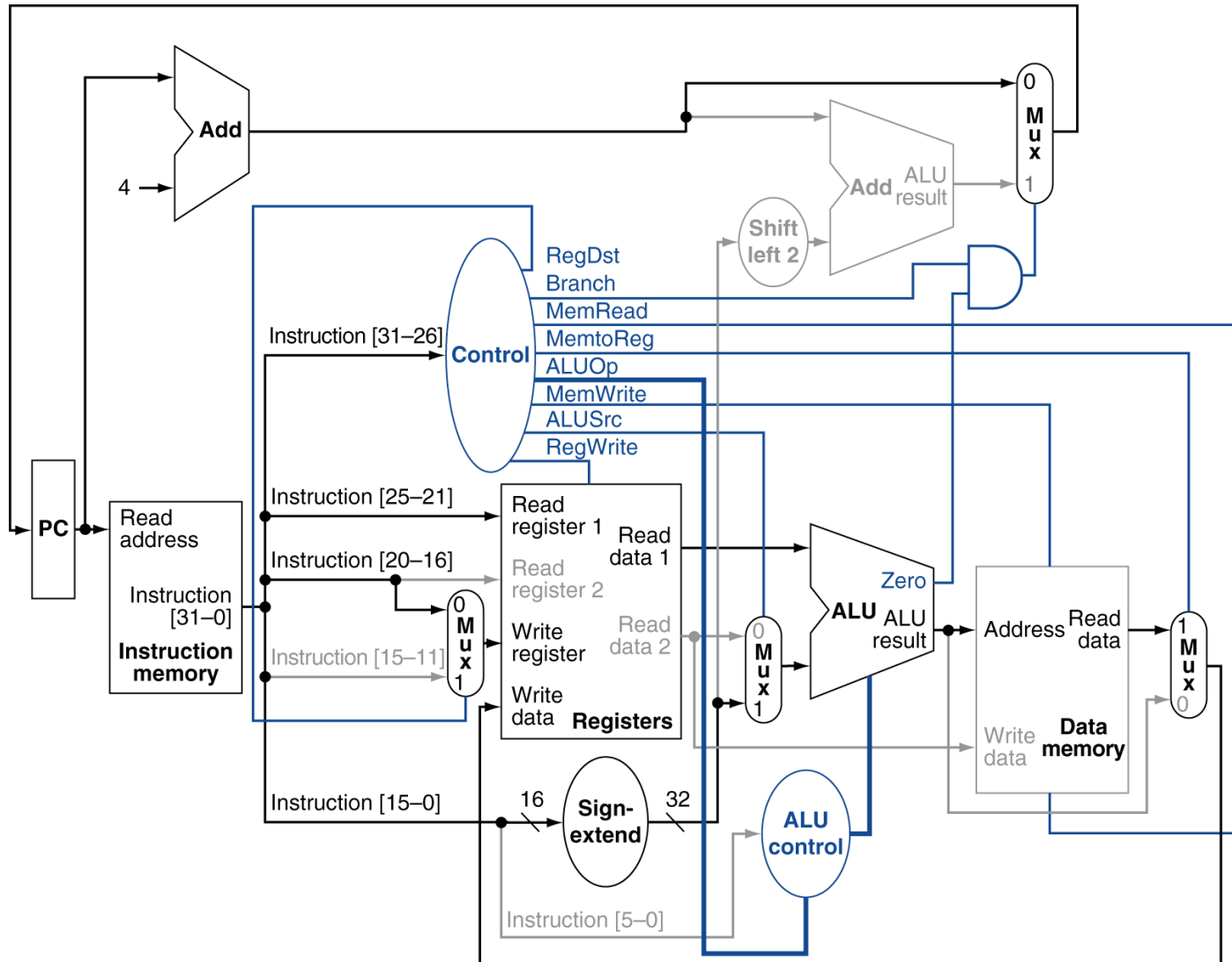

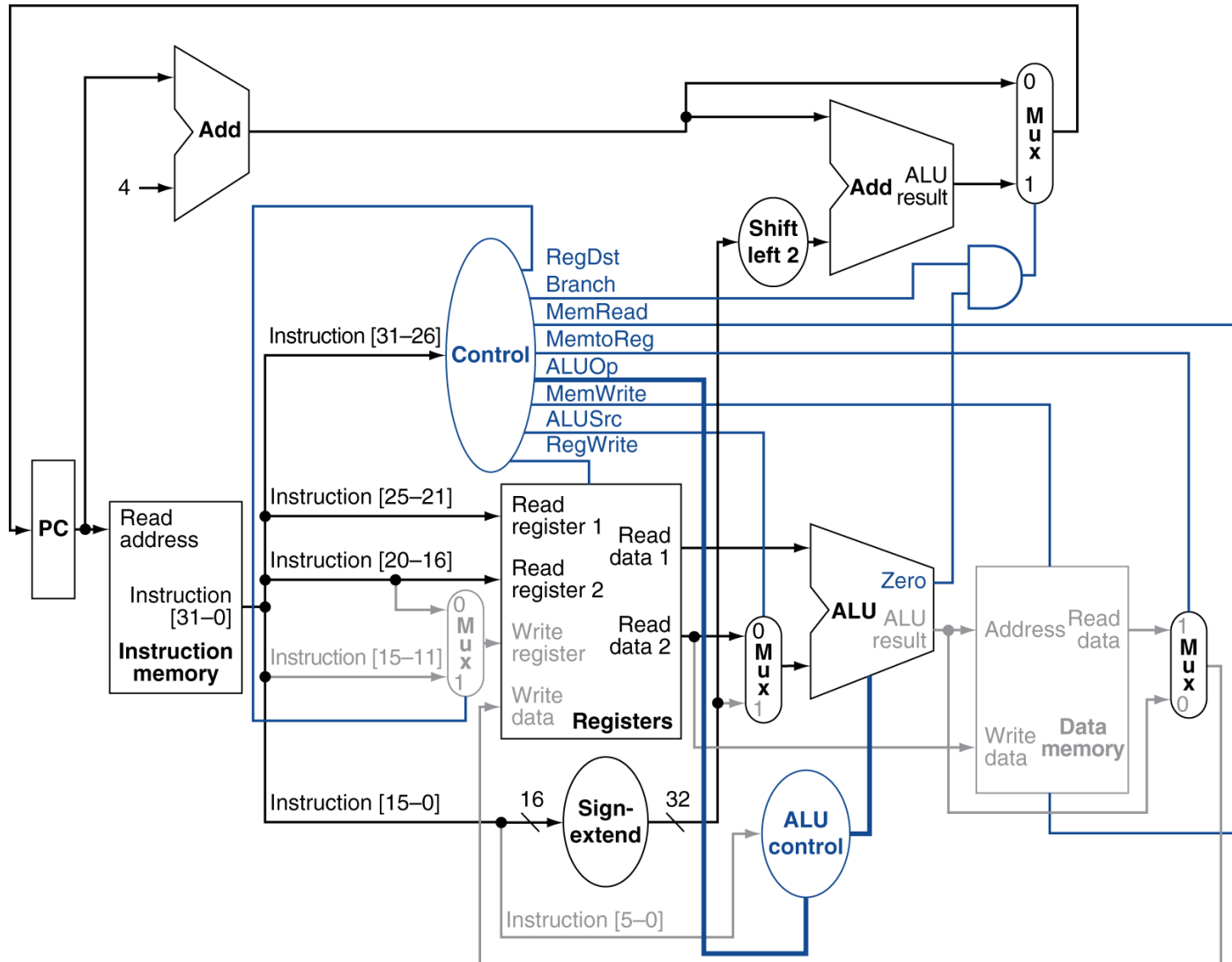


# Lecture 3: The Processor

## ■ J-Type Instruction

 

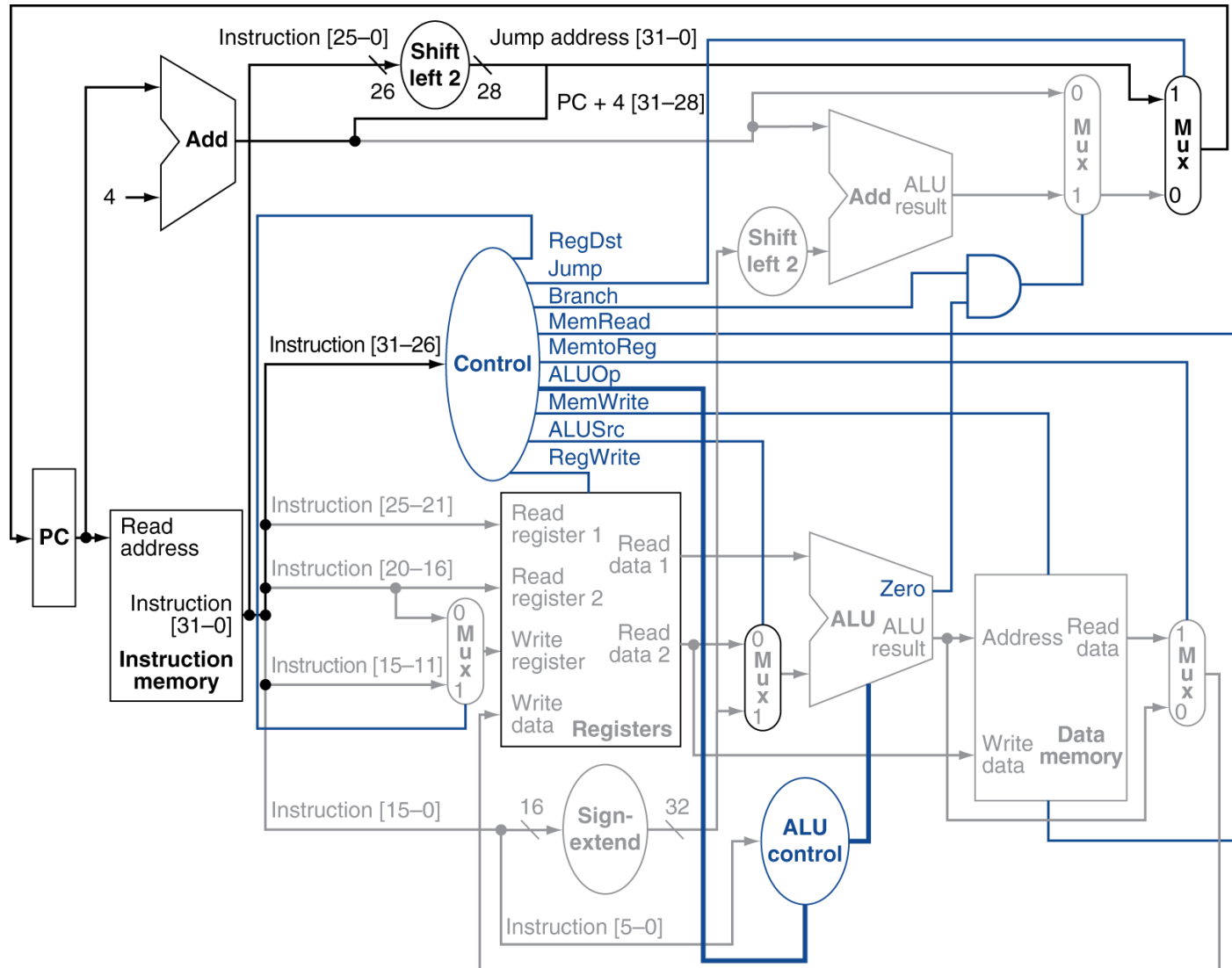- **Jump uses word address**
- **Update PC with concatenation of**
  - Top 4 bits of current PC+4 (bits 31:28)
  - 26-bit jump address
  - 00
- **Need an extra control signal decoded from opcode**



## Lecture 3: The Processor

### ■ Finalizing Control Circuit Design


- **Combinational Network**

	Inputs				Outputs								
Instruction	Opcode	funct	shamt	ALU func	ALUContrl	RegDst	Branch	JUMP	MemToReg	MemWrite	ALUsrc	RegWrite	zeroExt
LW	xxxxx			ADD	0010	0	0	0	1	0	1	1	0
SW	yyyyyy			ADD	0010	x	0	0	x	1	1	0	0
BEQ	zzzzz			SUB	0110	x	1	0	x	0	0	0	0
R-type	add	100000		ADD	0010	1	0	0	0	0	0	1	0
	sub	100010		SUB	0110	1	0	0	0	0	0	1	0
	and	100100		AND	0000	1	0	0	0	0	0	1	0
	or	100101		OR	0001	1	0	0	0	0	0	1	0
	shift	xxxx	xxxx	SHIFT		1	0	0	0	0	0	1	0
	ori					1	0	0	0	0	0	1	1
Jump					x	x	x	1	x	0	x	0	x

## Lecture 3: The Processor


 
### ■ Performance Issues

- Single Clock
  - Functional Block have different delays
  - Single clock designs use the clock inefficiently – the clock must be timed to accommodate the slowest instruction
  - Longest delay determines clock period
    - ✓ Critical path: load instruction
    - ✓ Instruction memory → register file → ALU → data memory → register file
  - Violates design principle: Making the common case fast
  - We will improve performance by pipelining



## Lecture 3: The Processor

### ■ Solution

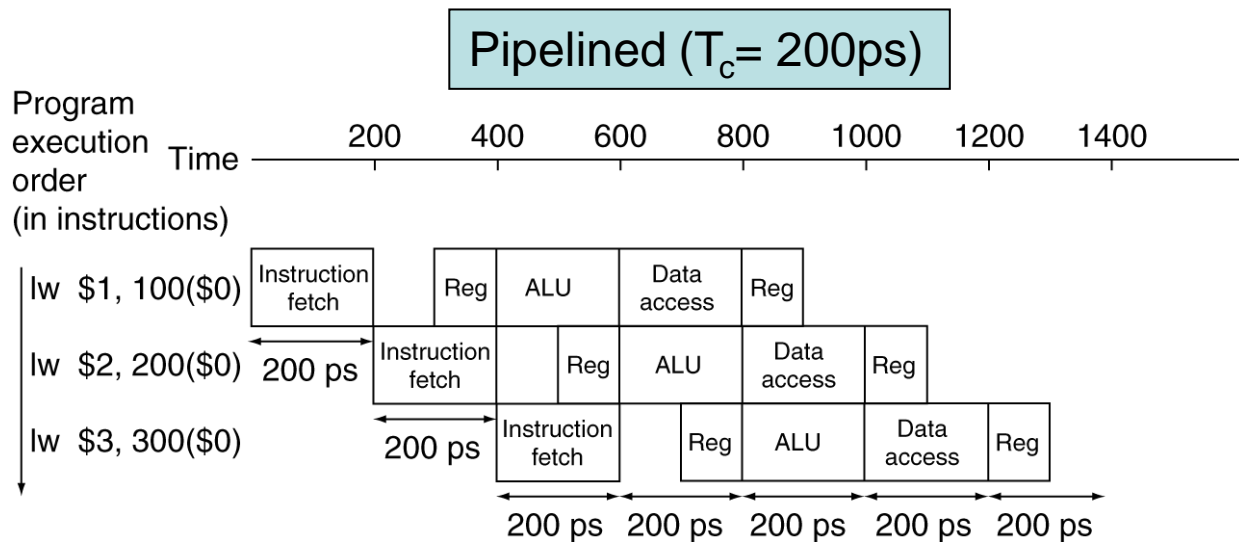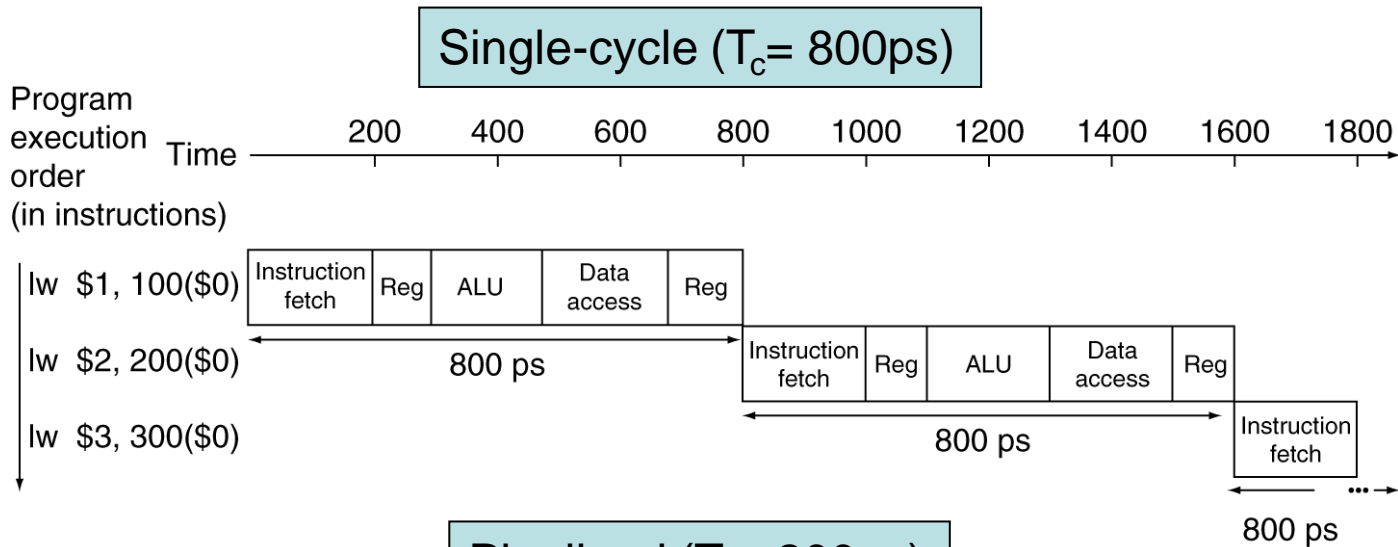



## Lecture 3: The Processor

---

- Next lecture
  - Multicycle datapath - Pipelining